

國立高雄應用科技大學  
107 學年度研究所碩士班招生考試  
電機工程系碩士班  
電路學(甲組)

試題 共 2 頁，第 1 頁

- 注意：a. 本試題共 五 題，每題 20 分，共 100 分  
b. 作答時不必抄題  
c. 考生作答前請詳閱答案卷之考生注意事項

1. For the circuit shown in Fig. 1, find the value of current  $i_a$  and the power absorbed by the dependent voltage source.

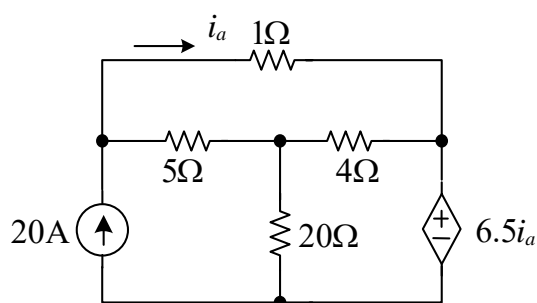


Fig. 1

2. In the circuit in Fig.2 the voltage and current expressions are

$$v = 32e^{-500t}V, \quad i = 8e^{-500t}mA, \quad t > 0$$

Find the time constant of this circuit and the values of R and C.

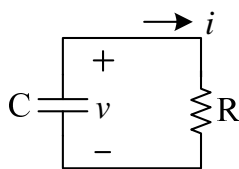


Fig. 2

【背面尚有試題】

3. In the circuit shown in Fig. 3, a load having an impedance of  $120+j90\ \Omega$  is fed from a voltage source through a line having an impedance of  $3+j4\ \Omega$ . The effective value of the source voltage is 465V and source frequency is 60Hz.
- (a) Calculate the average and reactive power delivered by the voltage source.
- (b) Calculate the size of the capacitor in microfarads that when connected in parallel with the load will make the load look purely resistive.

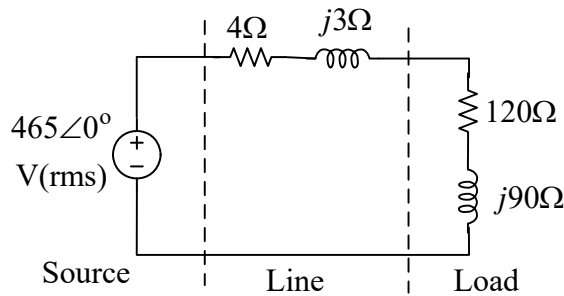


Fig. 3

4. If the switch in Fig. 4 has been closed for a long time before  $t = 0$  but is opened at  $t = 0$ .
- (a) Find the s-domain response  $I(s)$ .
- (b) Find the t-domain response  $i(t)$  for  $t \geq 0$ .

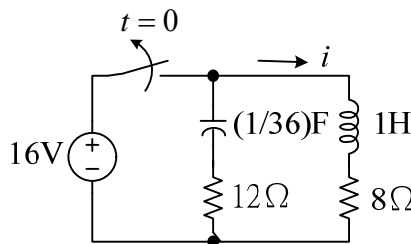


Fig. 4

5. A balanced  $\Delta$ -connected three-phase load has an impedance of  $Z_o = 85.5+j114\ \Omega/\phi$  as in Fig.5. The load is fed through a line having an impedance of  $Z_{line} = 1.5+j2.0\ \Omega/\phi$ . The phase voltage at terminal of the source is  $V_{an} = 250\angle 0^\circ\text{V(rms)}$ . The phase sequence is positive.
- (a) Calculate the line current  $I_{aA}$ .
- (b) Calculate the load terminal voltage  $V_{BC}$ .

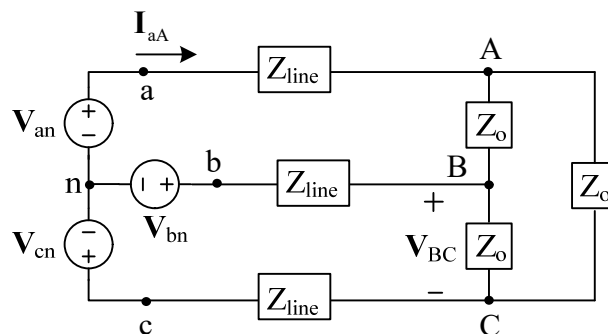


Fig. 5